

AC Power Analysis 3-Phase


Prepared for
Electrical Engineering Laboratory II, ECE L302

by

Mohammed Muthalib

Center for Electric Power Engineering
Drexel University

(<http://power.ece.drexel.edu>)

 

Outline

- Power Generation
- Fundamental Concepts (recap)
 - 1-Phase: V, I, S, P, Q, PF
- Balanced 3-phase
- Line-line vs. line-neutral voltage
- 3-phase power
 - $S_{3\Phi}$, $P_{3\Phi}$, $Q_{3\Phi}$
- Why 3-phase?
- This weeks experiment
- Power lab safety

Generation



Nuclear plant



Hydro plant




Coal plant




Fossil fuel plant

Generation

Conservation of energy

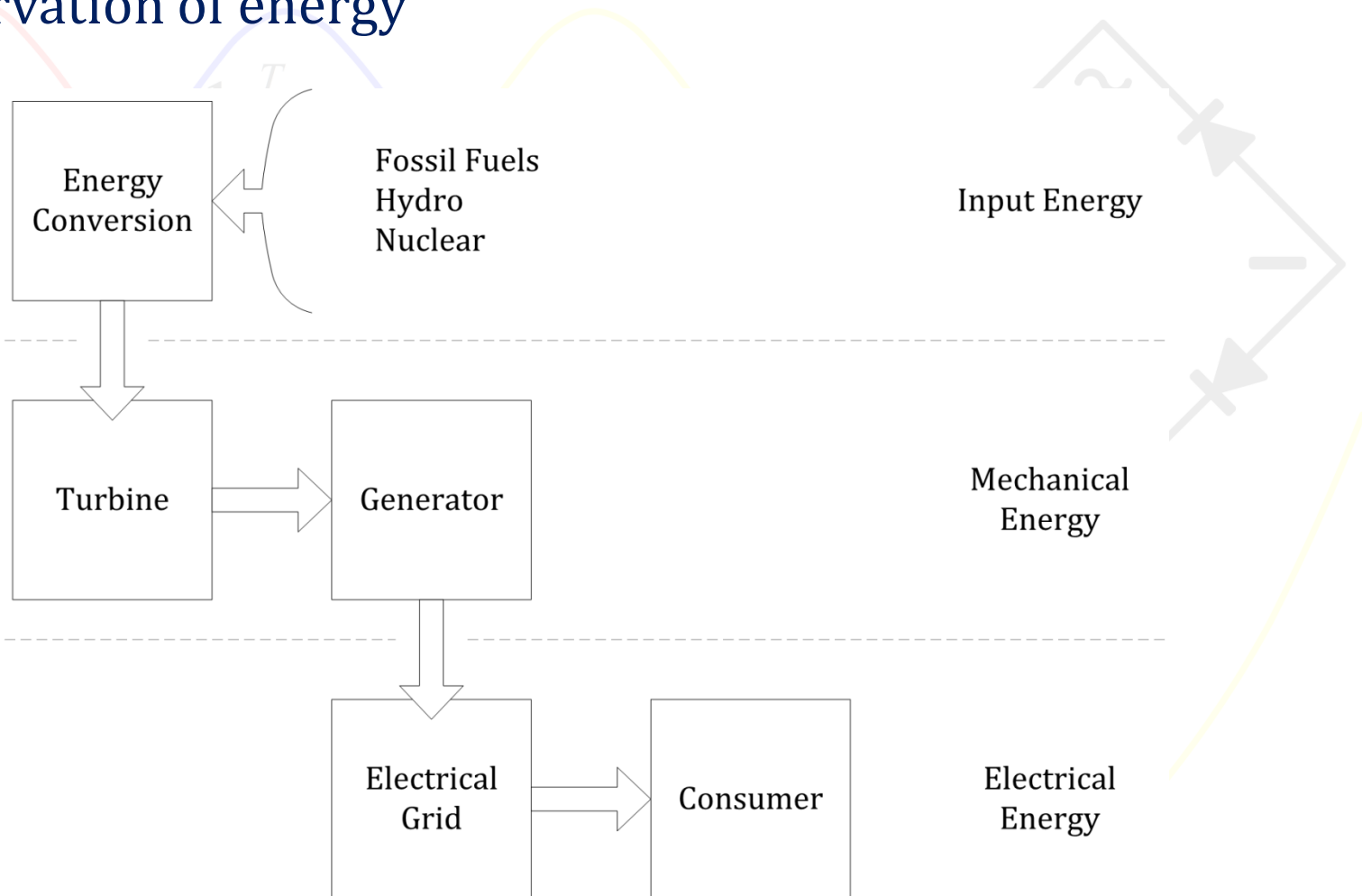

 

Generation

❑ Fossil Fuel:

- Burn fuel → Steam → Turbine → Generator

❑ Nuclear: $P = \frac{1}{T} \int p(t) dt$

- Nuclear reaction → Steam → Turbine → Generator

❑ Hydro:

- P.E. of reservoir → K.E. of water → Turbine → Generator

❑ Wind:

- K.E. of wind → rotational K.E. of blades in turbine → Generator

❑ Solar:

- Solar radiation → semiconductor energy transfer → Electron flow

❑ Solar and wind require storage and AC/DC conversion

Generation

□ Turbine – Generator

- Turbine provides mechanical torque to the rotor of the generator
- Stator has coils that react to the electro-magnetic field variations

 


Fig.3.10 Practical DC machine parts .

Generation

3-phase generation

- Stator has 3 coils wound 120° out of phase


 



Fig.3.10 Practical DC machine parts.

 

Phase A

Phase B

Phase C

 

ECE Department, University of Minnesota

<http://www.ece.umn.edu/users/riaz/animations/alternator.html>

Fundamental Concepts

□ AC voltage and current

- Sinusoidal time varying waveforms

$$v(t) = V_{\text{peak}} \sin(\omega t + \theta_v)$$

$$i(t) = I_{\text{peak}} \sin(\omega t + \theta_I)$$

θ_v –voltage phase angle

θ_I –current phase angle


- Phasor representation (time invariant)

$$\mathbf{V} = |\mathbf{V}| \angle \theta_v = |\mathbf{V}| e^{j\theta_v}$$

$$\mathbf{I} = |\mathbf{I}| \angle \theta_I = |\mathbf{I}| e^{j\theta_I}$$

Where $|\mathbf{V}|$ and $|\mathbf{I}|$ are rms values



$$V_{\text{peak}} \text{ (amplitude)} = \sqrt{2} |\mathbf{V}|$$

 

Voltage and current phasors
(polar coordinates)

Fundamental Concepts

Voltage and current waveforms

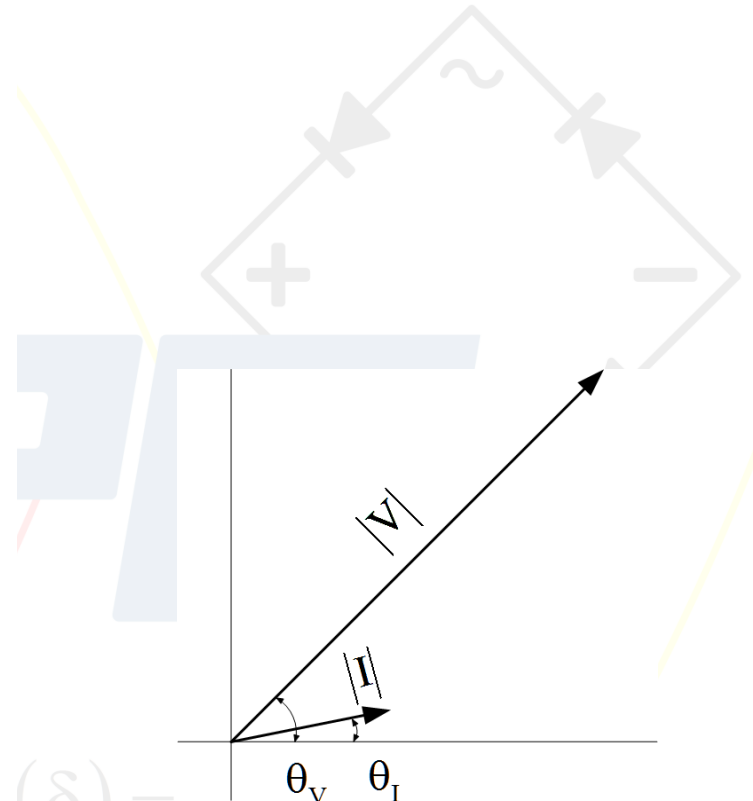 

Voltage and current phasors (polar coordinates)

Fundamental Concepts

□ Instantaneous power:

- Product of $v(t)$ and $i(t)$

$$v(t) = \sqrt{2} |V| \sin(\omega t + \theta_v)$$

$$i(t) = \sqrt{2} |I| \sin(\omega t + \theta_I)$$

$$p(t) = v(t) * i(t)$$

$$= 2 |V| |I| \sin(\omega t + \theta_v) \sin(\omega t + \theta_I)$$

use trigonometric identity


$$2 \sin u \sin v = \cos(u - v) - \cos(u + v)$$

$$u = \omega t + \theta_v, \quad v = \omega t + \theta_I$$

$$p(t) = |V| |I| \cos(\theta_v - \theta_I) - |V| |I| \cos(2\omega t + \theta_v + \theta_I)$$

time invariant
(constant)

time varying with
frequency 2ω

 


Fundamental Concepts

Instantaneous power

$$p(t) = v(t) * i(t)$$

$$P = \frac{1}{T}$$

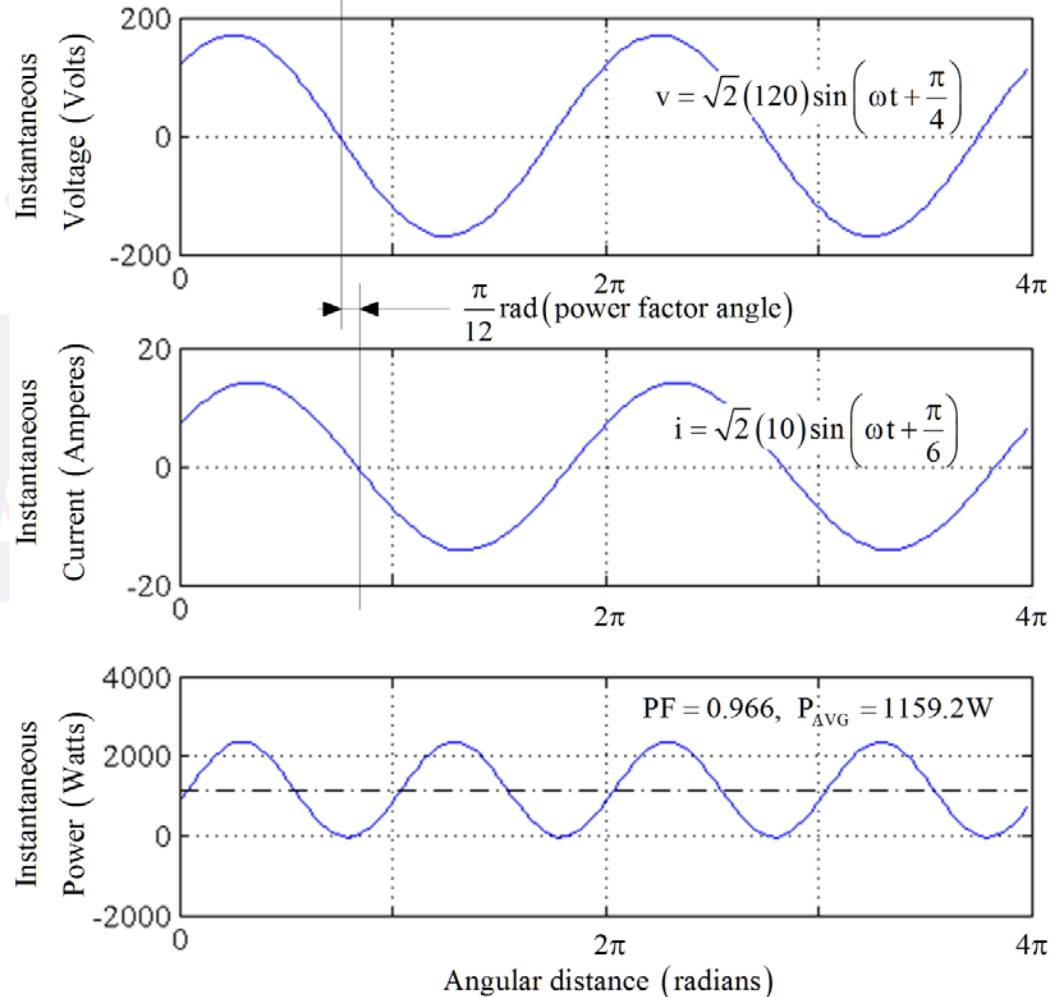

Fundamental Concepts

Complex power:

- Is a representation of power in a complex vector space
- Denoted S with units of VA

$$S = VI^* \text{ (*denotes complex conjugate)}$$


$$S = |V||I| \angle(\theta_v - \theta_i) = |V||I| e^{j(\theta_v - \theta_i)}$$


using Euler's formula

$$\begin{aligned} S &= |V||I| \cos(\theta_v - \theta_i) + j|V||I| \sin(\theta_v - \theta_i) \\ &= P + jQ \end{aligned}$$

- $|S|$ - apparent power

$$|S| = \sqrt{P^2 + Q^2} = |V||I|$$

 

 

Fundamental Concepts

□ Real power:

- Real power = Average power


$$P = P_{AVG} = |V||I|\cos(\theta_V - \theta_I)$$

- Denoted P with units of Watts
- Power absorbed by the resistive components of the system

□ Reactive power:

- Denoted Q with units of VAR
- Power absorbed by the reactive components of the system
- Example, Inductance and Capacitance

$$Q = |V||I|\sin(\theta_V - \theta_I)$$

 

Fundamental Concepts

□ Power Factor:

- Is a measure of how effectively a system component draws real power.
- It is the ratio between real power and apparent power



$$\text{PF} = \frac{P}{|S|} = \cos(\theta_V - \theta_I)$$


- PF is presented as a real number between 0 and 1 with a leading/lagging denotation for the PF angle
 - Lagging - current angle lags the voltage angle, $\theta_V > \theta_I$
 - Leading - current angle leads the voltage angle, $\theta_V < \theta_I$

Fundamental Concepts

□ Power Factor:

  - Which figure represents a load with a lagging PF?
 - What kind of load has a lagging power factor?
- Which figure represents a load with a leading PF?
 - What kind of load has a leading power factor?



 


Fundamental Concepts

- ❑ PF=1 indicates that all the power consumed in the system is real power.
 - A load with PF=1 emulates a resistor
 - Reactive power draw is zero
- ❑ Is PFC necessary? Why?

$$M\ddot{\delta} + D\dot{\delta} + P_G(\delta) = P_M^0$$

Fundamental Concepts

❑ PFC by injecting reactive power

 

$$S_{\text{new}} = P + jQ_{\text{new}} = P + j(Q - Q_{\text{correction}})$$

$$\cos(\theta_{\text{VI}}) < \cos(\theta_{\text{VI,new}})$$


❑ Reactive power injection is done by adding capacitive and inductive loads to the system.

- Capacitive – supply reactive power
- Inductive – consume reactive power

Balanced 3-phase

□ Balanced 3-phase circuit

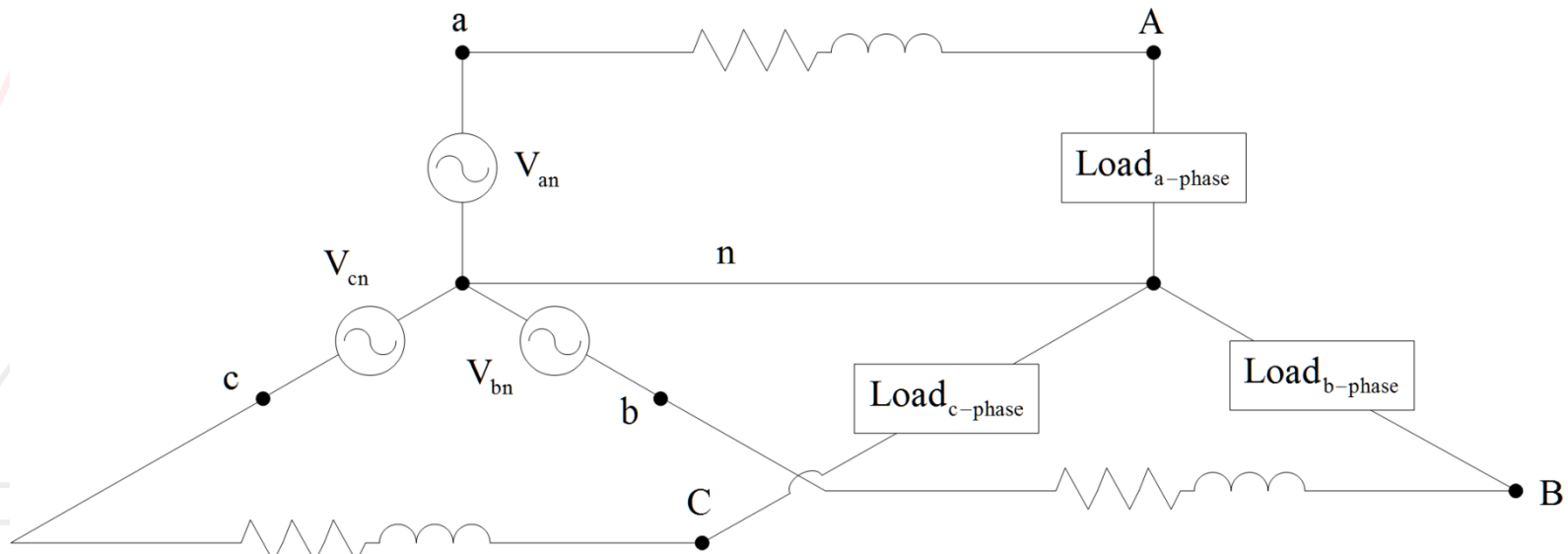- All components, loads, lines, etc. are assumed to be identical






- Balanced 3 Φ circuits are analyzed through a single phase equivalent analysis

Balanced 3-phase

Balanced 3-phase voltages

$$P = \frac{1}{T} \int p(t) dt$$

   

$$V_{an} = \sqrt{2} |V_{an}| \sin(\omega t + 0^\circ) \quad \text{Volts}$$

$$V_{bn} = \sqrt{2} |V_{an}| \sin(\omega t - 120^\circ) \quad \text{Volts}$$

$$V_{cn} = \sqrt{2} |V_{an}| \sin(\omega t + 120^\circ) \quad \text{Volts}$$

$$I_a = \sqrt{2} |I_a| \sin(\omega t + \theta_I + 0^\circ) \quad \text{Amps}$$


$$I_b = \sqrt{2} |I_a| \sin(\omega t + \theta_I - 120^\circ) \quad \text{Amps}$$

$$I_c = \sqrt{2} |I_a| \sin(\omega t + \theta_I + 120^\circ) \quad \text{Amps}$$

Line-line voltage

□ Line-line voltage

 - Voltage measure between phases, V_{ab} , V_{bc} , V_{ca}



$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} \\ &= V_{an} + (-V_{bn}) \end{aligned}$$

$$\begin{aligned} |V_{ab}| &= |V_{an}| \cos(30^\circ) + |V_{bn}| \cos(30^\circ) \\ &= \sqrt{3} |V_{an}| \end{aligned}$$

$$\angle V_{ab} = \angle V_{an} + 30^\circ$$

Example:

$$V_{an} = 120 \angle 0^\circ \quad \text{V}$$

$$V_{bn} = 120 \angle -120^\circ \quad \text{V}$$

$$V_{ab} = 208 \angle 30^\circ \quad \text{V}$$

3-phase power

Real Power

- $P_{3\Phi} = P_A + P_B + P_C$

$$P_A = |V_A| |I_A| \cos(\theta_{V,A} - \theta_{I,A}) \text{ Watts}$$

$$P_B = |V_B| |I_B| \cos(\theta_{V,B} - \theta_{I,B}) \text{ Watts}$$

$$P_C = |V_C| |I_C| \cos(\theta_{V,C} - \theta_{I,C}) \text{ Watts}$$

$$\theta_{V,B} = \theta_{V,A} - 120^\circ, \quad \theta_{I,B} = \theta_{I,A} - 120^\circ$$


$$\theta_{V,C} = \theta_{V,A} + 120^\circ, \quad \theta_{I,C} = \theta_{I,A} + 120^\circ$$

$$|V_A| = |V_B| = |V_C|, \quad |I_A| = |I_B| = |I_C|$$

$$P_B = |V_A| |I_A| \cos((\theta_{V,A} - 120^\circ) - (\theta_{I,A} - 120^\circ))$$

$$= |V_A| |I_A| \cos(\theta_{V,A} - \theta_{I,A})$$

$$= P_A$$

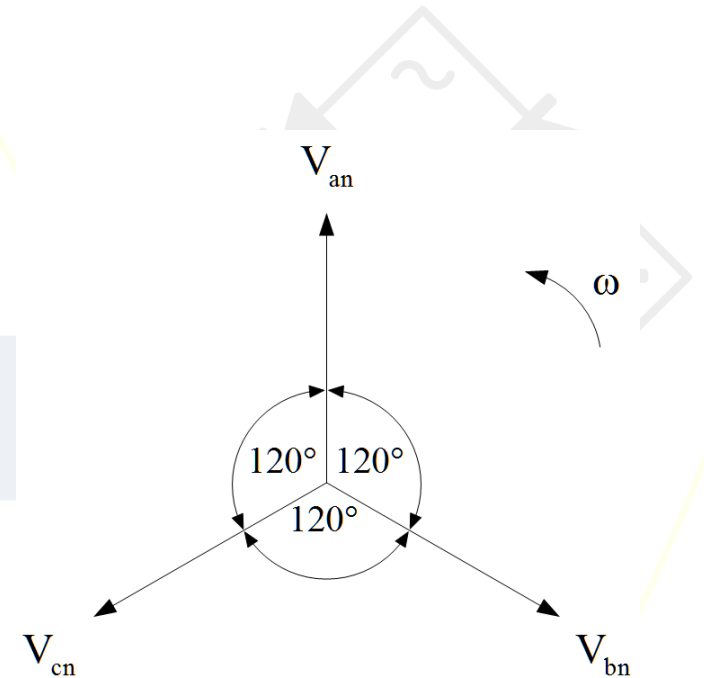

Balanced 3-phase voltage phasor

3-phase power

Real Power

$$P_{3\Phi} = P_A + P_B + P_C \quad \text{Watts}$$

$$P_{3\Phi} = 3|V_{an}||I_a|\cos(\theta_{V,A} - \theta_{I,A}) \quad \text{Watts}$$

$$P_{3\Phi} = \sqrt{3}|V_{LL}||I_L|\cos(\theta_{V,A} - \theta_{I,A}) \quad \text{Watts}$$

Reactive power

$$Q_{3\Phi} = Q_A + Q_B + Q_C \quad \text{VAr}$$

$$Q_{3\Phi} = 3|V_{an}||I_a|\sin(\theta_{V,A} - \theta_{I,A}) \quad \text{VAr}$$


$$Q_{3\Phi} = \sqrt{3}|V_{LL}||I_L|\sin(\theta_{V,A} - \theta_{I,A}) \quad \text{VAr}$$

Complex Power

$$S_{3\Phi} = 3V_A (I_A)^* \quad \text{VA}$$

$$S_{3\Phi} = P_{3\Phi} + jQ_{3\Phi} \quad \text{VA}$$


$$|V_{LL}| = |V_{ab}| = \sqrt{3}|V_{an}|$$

 

Balanced 3-phase voltage phasor

Why 3-phase?

 - ❑ Electrical energy has to be transmitted/distributed over long distances
 - Cables are heavy (engineering problem to string up in the air) and lossy



https://www.osha.gov/SLTC/etools/electric_power/illustrated_glossary/transmission_lines.html

Why 3-phase?

□ Neutral Current (balanced 3-Φ)

$$I_a = \sqrt{2} |I_a| \angle (\theta_I + 0^\circ) \text{ Amps}$$

$$I_b = \sqrt{2} |I_a| \angle (\theta_I - 120^\circ) \text{ Amps}$$

$$I_c = \sqrt{2} |I_a| \angle (\theta_I + 120^\circ) \text{ Amps}$$

$$I_n = I_a + I_b + I_c$$


$$= \sqrt{2} |I_a| (\cos(\theta_I) + \cos(\theta_I - 120^\circ) + \cos(\theta_I + 120^\circ))$$


$$+ j\sqrt{2} |I_a| (\sin(\theta_I) + \sin(\theta_I - 120^\circ) + \sin(\theta_I + 120^\circ))$$

$$= \sqrt{2} |I_a| (\cos(\theta_I) + 2\cos(\theta_I)\cos(-120^\circ))$$

$$+ j\sqrt{2} |I_a| (\sin(\theta_I) + 2\sin(\theta_I)\cos(-120^\circ))$$

$$= 0$$

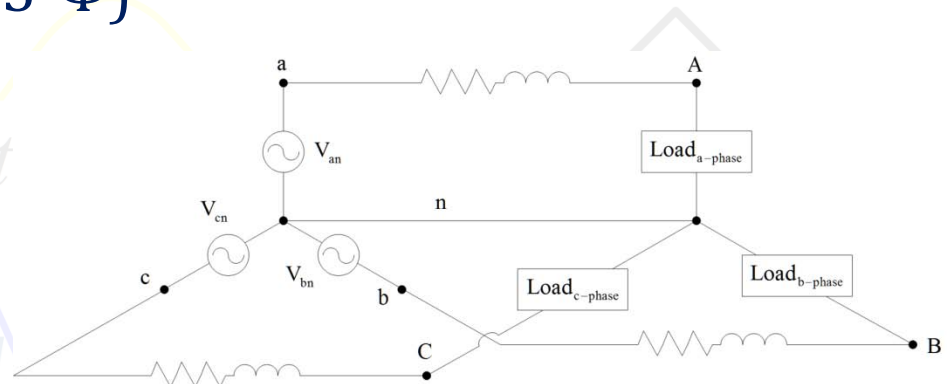

 


Why 3-phase?

- ❑ Transmission of power in balanced 3-phase can be done without a neutral conductor
- ❑ More efficient and economical since:
 - less losses from conductor
 - Less cost with respect to material and construction
- ❑ NOTE:
 - Distribution systems are unbalanced and require a neutral conductor
 - Connect back to local electrical substations
 - Supplied through distribution transformers

$$M\delta + D\delta + P_G(\delta) = P_M^0$$

Electrical Supply

Transmission/Distribution


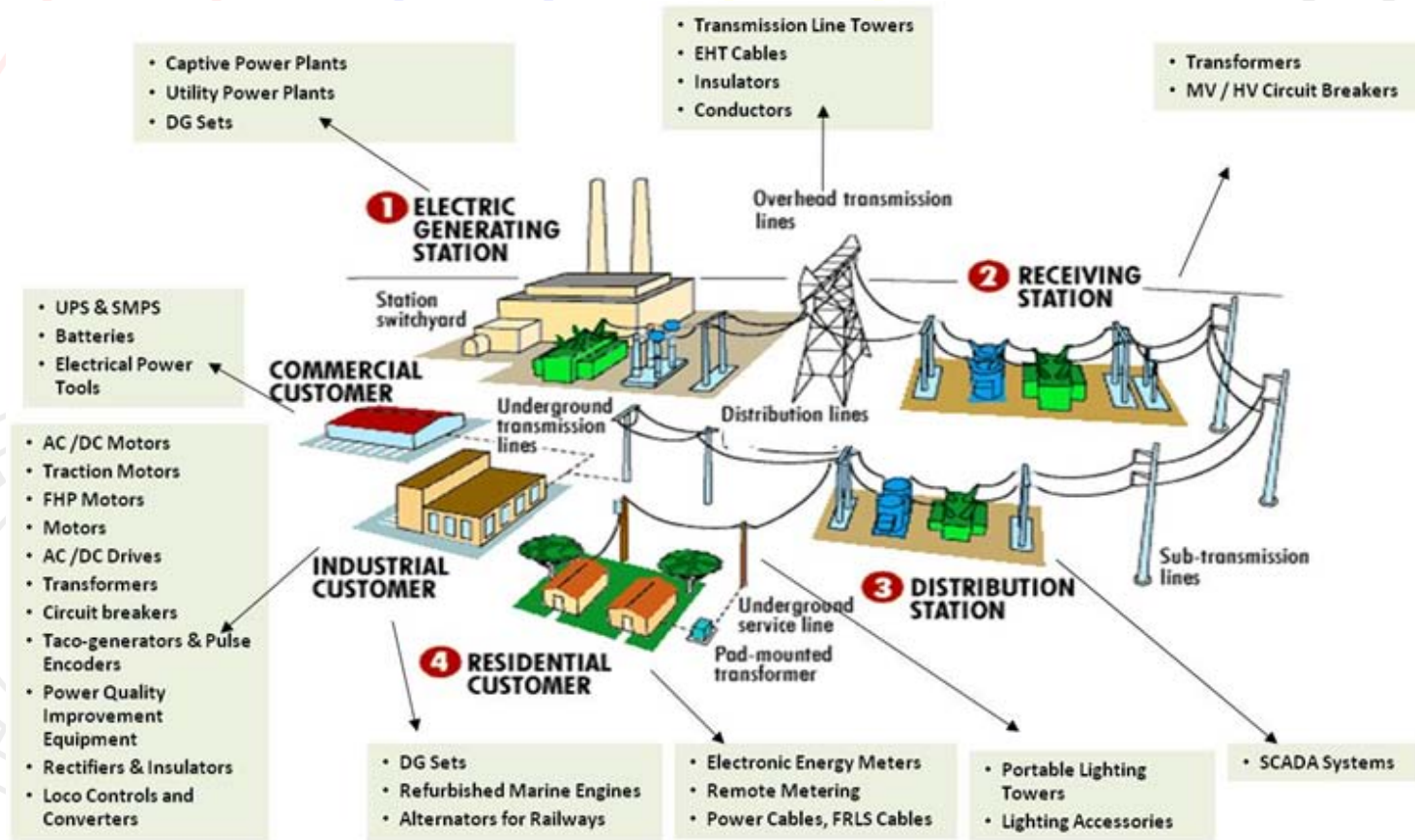


<http://www.avalon-energy.com/sample.aspx?C1=28>

Electrical Supply

Residential connection


$$P = \frac{1}{T} \int_0^T p(t) dt$$

  

<http://waterheatertimer.org/See-inside-main-breaker-box.html>

Lab Experiment

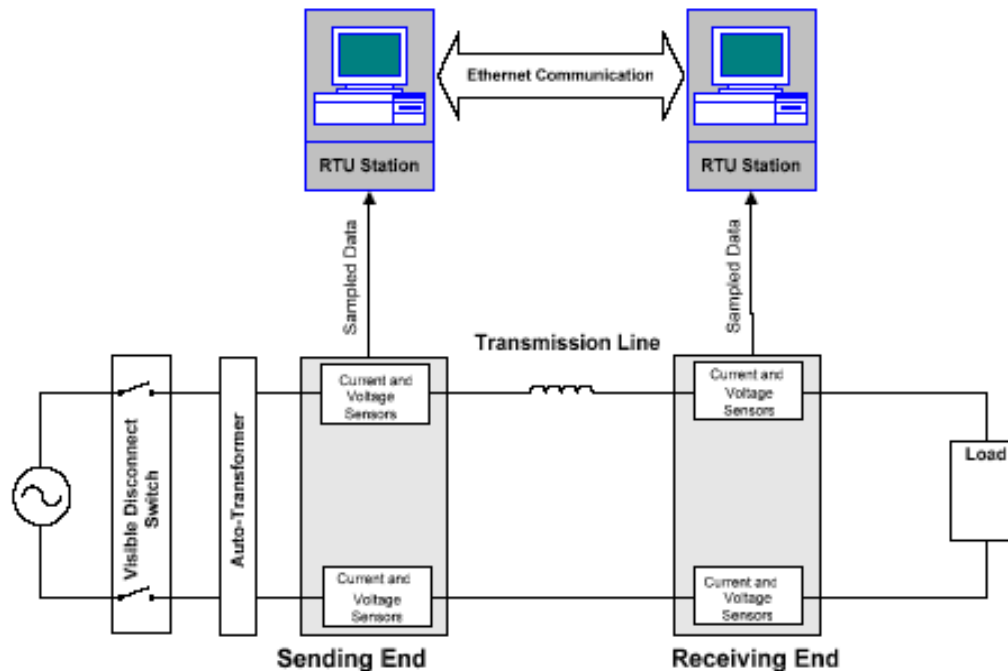
- ❑ Simulating a 2-bus power system (Transmission)
- ❑ Measure voltages and currents; calculate power
- ❑ Observe effects of loading




Lab Experiment

□ Test system with 3 load types

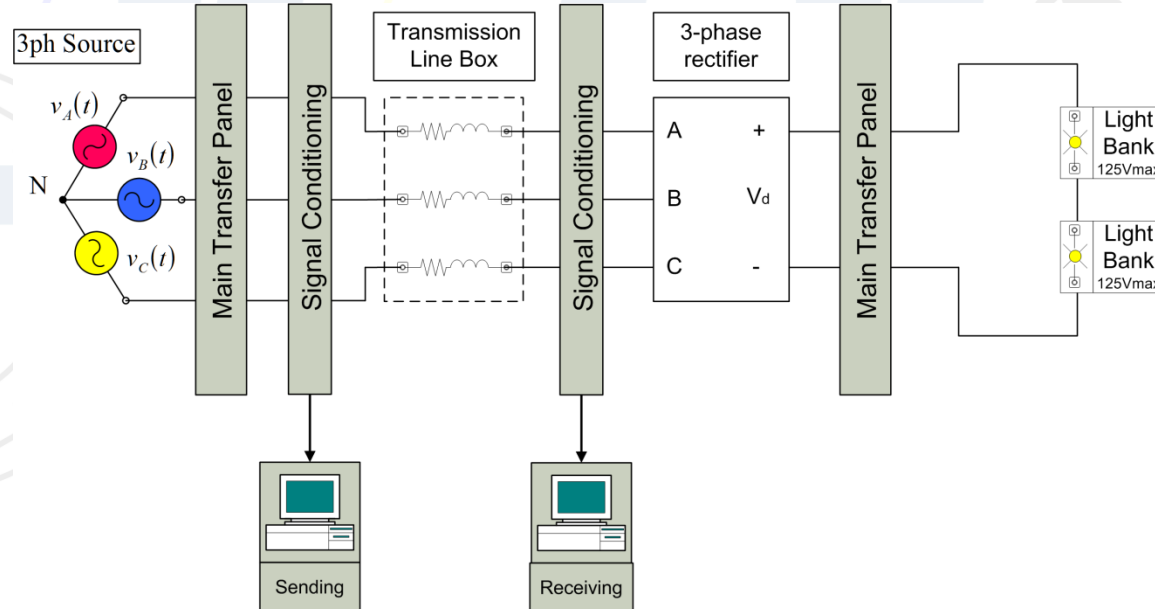- Resistive Load (4 – 20 bulbs)
- RL (20 bulbs + 0 - 5 inductors)
- RC (20 bulbs + 0 - 4 capacitors)
- Nonlinear Load



 

Lab safety

- You will be dealing with voltages and currents of 120V and 25A
- Adherence to safety and conduct guidelines is imperative
- Please read the Power Lab Safety document
- Please watch lab safety video
 - <http://power.ece.drexel.edu/videos/>

$$M\ddot{\delta} + D\dot{\delta} + P_G(\delta) = P_M^0$$

$$P = \frac{1}{T} \int_0^T p(t) dt$$

Thank you

Questions are most welcome

$$M\ddot{\delta} + D\dot{\delta} + P_G(\delta) = P_M^0$$